

Name:

ID:

Section:

Q-1: Draw the I-V characteristics curve for both circuits:

[3+3]

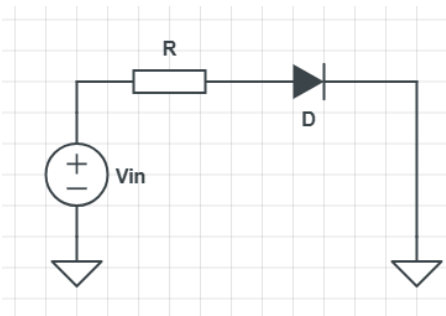


Figure 1


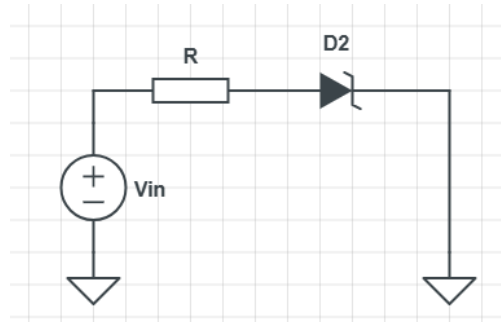


Figure 2


Q-2: Answer the following questions-

- i. Draw V_{out} (Input: 10V sinusoidal AC)
- a.


[4+4+5+4]

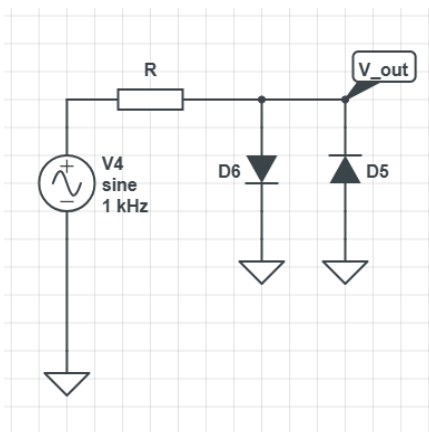


b.

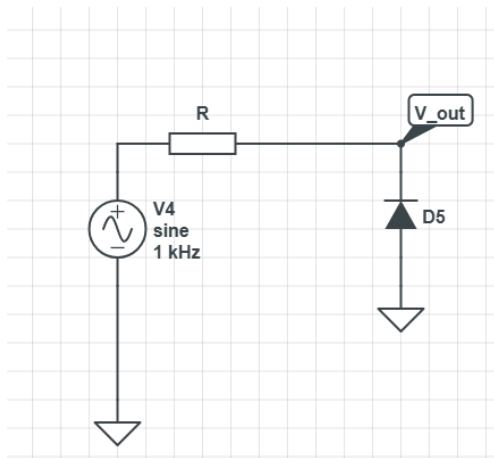

c.

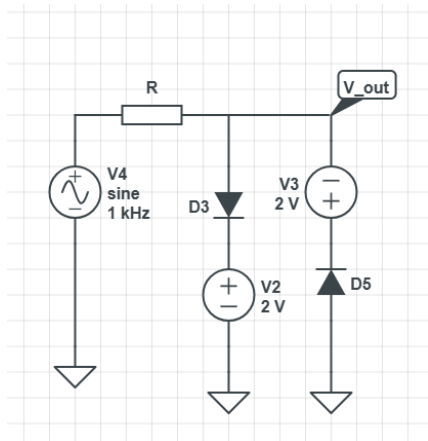

d.

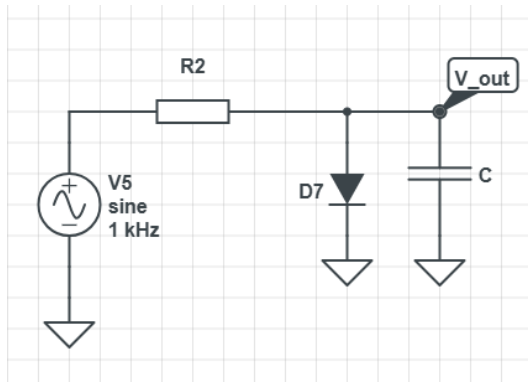

ii. For the circuit of problem- (i.d), what impact does capacitor value have on the circuit?


[3]

Q-3: For the full wave rectifier circuit, the values of diode voltages when in forward are:

[5]

$V_{D1}=0.76V$, $V_{D2}=0.7V$, $V_{D3}=0.80V$ and $V_{D4}=0.72V$.

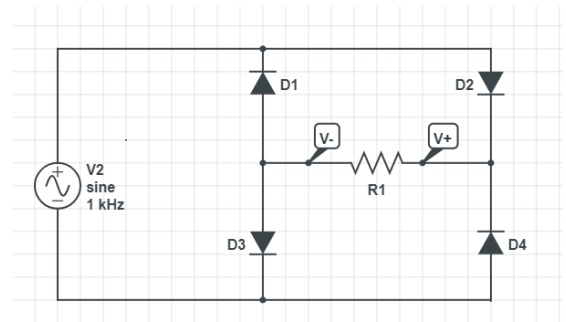Calculate the maximum output voltage (across the resistor) for both positive and negative half cycle.



Q-4:

[9]

- a) If an input signal has 1000Hz frequency and the time per division of the digital oscilloscope was set at .25ms/div, how many horizontal unit/divisions will be required to display a full cycle of the signal?
- b) What do you mean by 20p-p sine AC wave?
- c) How many types of AC wave can be generated by using function generator?
- d) When you are provided a Zener diode from a box written $V_Z=5.6V$ on it, what do you understand by the value of V_Z ?
- e) If volt/div= 1V/div, then how many vertical divisions will be needed to display a full cycle of 16V p-p square wave?
- f) What is the minimum number of diodes needed to build a both-sided clipper circuit?